


CSED 311 Computer Architecture (2021)

Introduction to Verilog

Sungjun Cho

What is Verilog?

 
- One of **Hardware Description Languages** (HDL)
 - **Describe** how hardware is constructed
 - Verilog implements **register-transfer-level** (RTL) abstractions



Describe how information flows **from register to register**

What is Verilog?

 - One of **Hardware Description Languages** (HDL)
 - **Describe** how hardware is constructed
 - Verilog implements **register-transfer-level (RTL)** abstractions




Describe how information flows **from register to register**




What is Verilog?

 - One of **Hardware Description Languages** (HDL)
 - **Describe** how hardware is constructed
 - Verilog implements **register-transfer-level** (RTL) abstractions



 
Describe how information flows **from register to register**



Verilog module


- Modules are the building blocks of Verilog designs
 - Similar to functions in the programming language
- Modules are defined by port declarations (I/O) and Verilog code (implementation)
 - Port declarations => similar function arguments in the programming languages
 - Verilog code => functionality
- Currently, recommend to write **a module** in **a file** ended with .v
 - Modularization
 
```
full_adder.v  
  
module full_adder (input x, input y, input cin,  
                  output s, output cout);  
    // Verilog code  
endmodule
```




Verilog module I/O ports

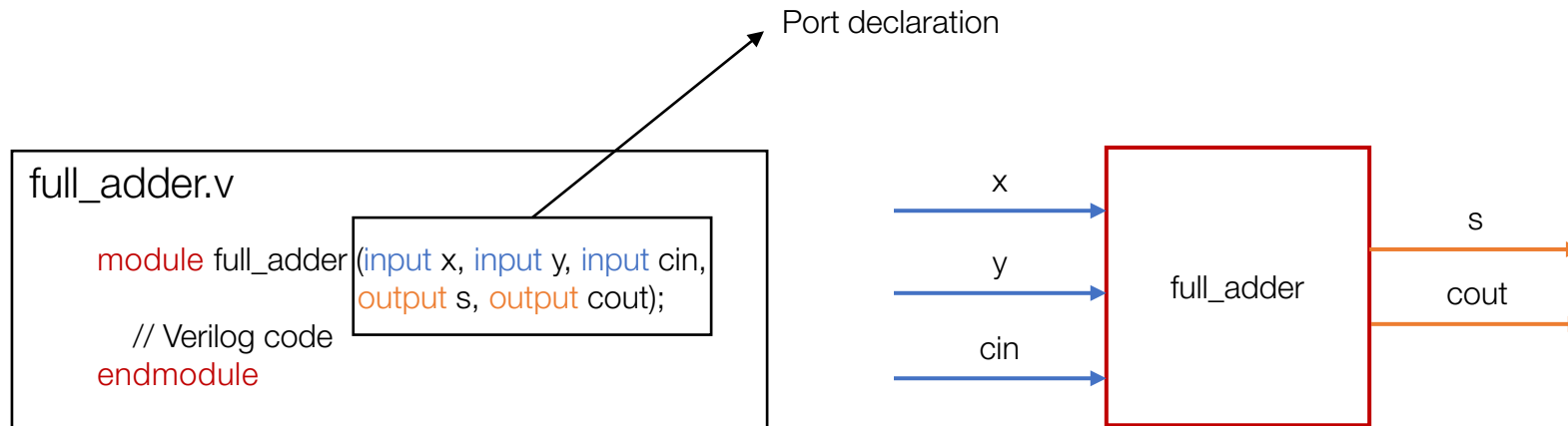- Ports are the interface between a module and its environment
 - Environment
 - Something that generates information flow that goes to the module
 - Something that receives the information flow generated by the module
- Each port has a name and a type
 - input
 - output
 - inout
 - output reg



Top-level module

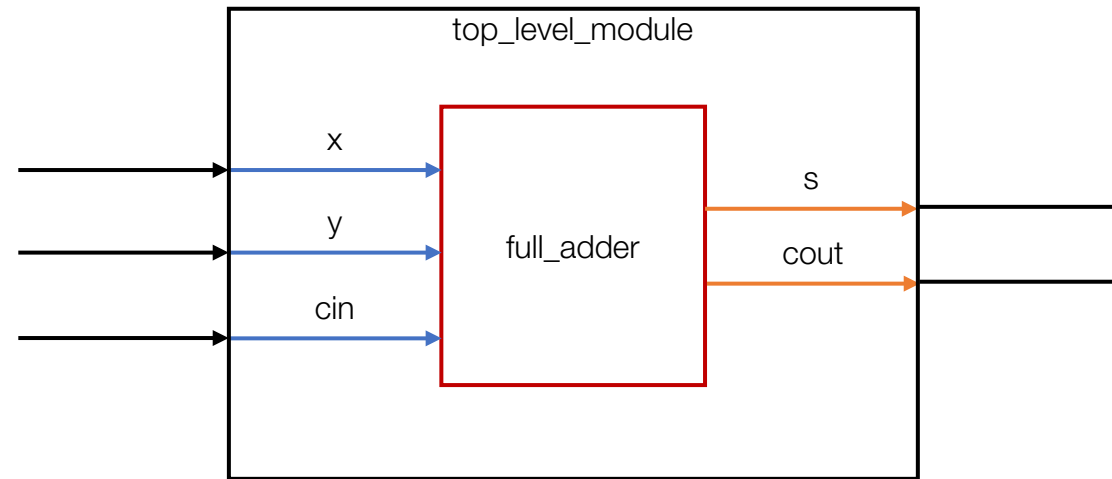- Every Verilog design has a **top-level module**
 - **The highest** level of the design hierarchy => Similar to the **main function** in the programming languages
- Modules defined by the designer are instantiated within the top-level module
 - General modules also can instantiate other modules



Module instantiation


- You have two files
 - top_level_module.v
 - full_adder.v

full_adder.v

```
module full_adder (input x, input y, input cin,  
                  output s, output cout);  
    // Verilog code  
endmodule
```

top_level_module.v
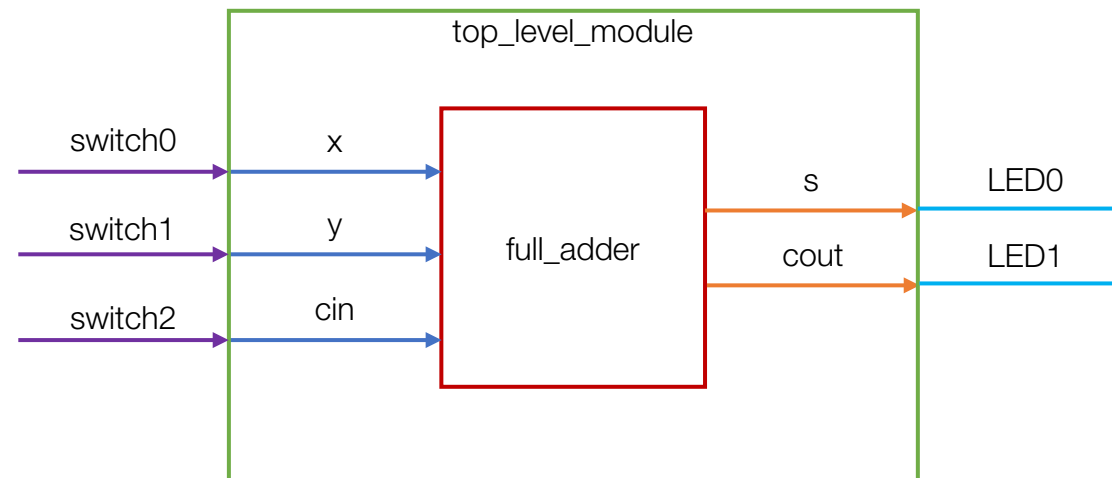
```
module top_level_module (input switch0, input switch1, input switch2,  
                        output LED0, output LED1);  
    // Verilog code  
    // instantiate full_adder()  
    // module_name instance_name  
    full_adder my_adder(  
        .x(switch0),  
        .y(switch1),  
        .cin(switch2),  
        .s(LED0),  
        .cout(LED1));  
endmodule
```



Wire

- Wires (also called nets) are analogous to wires in a circuit
 - Wire transmits values between inputs and outputs

```
wire a; // 1 bit wire  
wire b; // 1 bit wire
```

- Vector (multiple bit widths) wires
 - Vectors can be declared at [high# : low#] or [low# : high#]
 - The left number is always MSB of the vector => [MSB bit index : LSB bit index]


```
wire [31 : 0] a; // 32 bit wire  
wire [63 : 0] b; // 64 bit wire (Bit at 63 is MSB)  
wire [0 : 63] c; // 64 bit wire (Bit at 0 is MSB)
```



Wire

- To use vector wires (multiple bitwidth) for declaring ports in a module:
 
```
module two_bit_adder (input [1 : 0] x, input [1 : 0] y,  
                     output [2 : 0] z);  
    // Implement two bits adder here  
endmodule
```



Reg

- Reg is required whenever the state (or value) must be preserved.
 - `reg [31 : 0] x; // 32-bit reg`
 - `reg x; // 1-bit reg`
- Reg is used to assign the value in an `always block` (procedural assignment).
 - Or, can be used in structured procedure
 - Discussed later

Array

- Wires and regs can be declared as an array

- An array of wire

`wire [7 : 0] wire_array [5 : 0];` // declare an array of 8-bit vector wire. The length of array is 6.

- An array of reg (Note that this usually represents the memory!)

`reg [31 : 0] memory [0 : 1023];` // declare an array of 32-bit vector reg. The length of array is 1024.

- To access an array:

`memory[15][23 : 0] = 0;` // [15] represents the index of an array. [23 : 0] accesses the bits from 23 to 0.

- An array also can be declared as a multi-dimensional array
 - E.g., `reg [31 : 0] memory [0:1024][0:512][0:256]` // three-dimensional array

Verilog literals

- Syntax: [bit width]'[radix][literal]
 - Radix can be **d** (decimal), **h** (hexadecimal), **o** (octal), **b** (binary)
 - **2'****d**1 : **2-bit** literal (**decimal** 1)
 - **16'****h**AD14 : **16-bit** literal (**hexadecimal** 0xAD14)
 - **8'****b**01011010 : **8-bit** literal (**binary** 0b01011010)
 - **8**{**4'****b**0101} : **32-bit** literal (replicating 4'b0101) (**binary** 0b01010101...0101)

Verilog macros

- Macros in Verilog are similar to macros in C
- ``include`
 - Include a Verilog source file at specified location
- ``define <constant name> <constant value>`
 - Declare a synthesis-time constant
 - To use defined value: ``<constant name>`

constants.v

```
`ifndef CONSTANTS_V
`define CONATANTS_V

`define ADDR_BITS 16
`define NUM_WORDS 32
`endif
```

design.v

```
`include "constants.v"

module memory(input [ADDR_BITS - 1 : 0] addr,
              output ...);
    // implementation
endmodule
```

Verilog module parameterization

- Similar to macros, Verilog provides a way to declare constant parameter for the module.
 - Useful to define the width of bus or others

```
module adder #(parameter data_width = 32) (  
    input [data_width - 1 : 0] a,  
    input [data_width - 1 : 0] b,  
    output [data_width : 0] c);  
    assign c = a + b;  
endmodule
```

```
module top();  
    localparam adder1width = 64; // can be used only for the module, top()  
    localparam adder2width = 32; // can be used only for the module, top()  
    reg [adder1width - 1 : 0] a, b;  
    reg [adder2width - 1 : 0] c, d;  
    wire [adder1width : 0] out1;  
    wire [adder2width : 0] out2;  
    adder #(.data_width(adder1width)) adder64 (.a(a), .b(b), .s(out1));  
    adder #(.data_width(adder2width)) adder32 (.a(c), .b(d), .s(out2));  
endmodule
```

Modeling

- Three ways to design the hardware:
 - Gate-Level modeling => low-level modeling (painful)
 - Dataflow modeling
 - Behavioral modeling
- } The term RTL design is used for a combination of these two.
- We will learn dataflow modeling and behavioral modeling

Dataflow modeling

- Continuous (dataflow) assignment
 - Drive a value onto a net (wire or reg)
 - A simple and natural way to represent combinational logic
 - Declare before use

```
module example (input [1 : 0] x, input [1 : 0] y,  
               output [1 : 0] z, output [2 : 0] f)  
    // assign z = x & y;  
    // assign f = x + y; this implements two bits adder  
endmodule
```

```
module example (input [1 : 0] x, input [1 : 0] y, input a,  
               output [1 : 0] z)  
    // assign z = a ? x : y; conditional operator (multiplexer)  
endmodule
```

```
wire [7 : 0] a; // 8 bit wire  
wire [31 : 0] b; // 32 bit wire  
wire [31 : 0] c; // 32 bit wire  
wire [5 : 0] d; // 6 bit wire
```

```
// assign d = a[5 : 0]; // bit slicing  
// assign c = {a, b[25: 2]}; // concatenation + bit slicing  
// assign c = { 32{d[2]} }; // replicating d (bit at 3) 32 times => 32 bits  
// assign {a[5], b[2 : 1]} = c[23:21]; // assign the sliced value to concatenated net
```

```
module example (input [1 : 0] x, input [1 : 0] y, input a,  
               output [1 : 0] z)  
    // Assignment 1  
    // wire [1 : 0] out;  
    // assign out = x | y;  
    // assign z = out;  
  
    // Assignment 2, directly assign the input to the wire  
    // wire [1 : 0] out = x | y;  
    // assign z = out;  
  
endmodule
```

Bits are truncated if not matched or filled with zeros

- Why 'continuous' ?
 - Right-hand expression is **continuously** evaluated whenever the values are changed

Behavioral modeling

- Two structured procedure statements in Verilog
 - always
 - Initial
- **Initial** statements are executed **only once at the beginning of simulation**.
 - Initial statement is not synthesizable, it only works for simulation.
 - Usually used to initialize values and used for test benches.
- **Always** statements are **continuously** executed.
 - Used to model a block of activity that is repeated continuously in a digital circuit.
 - Do not think 'always' as 'while' loop in programming languages.
 - Code in 'always' is a continuously repeated activity in a digital circuit until 'power off' occurs.

Behavioral modeling

- How to design clock generator by using **initial** and **always** statements

```
`timescale 1ns/10ps

module clock_generator (output reg clock);

    // initialize the value of 'clock'.
    // 'initial' statement is executed only at the beginning of the simulation (time 0).
    initial begin
        clock = 1'b0;
    end

    // toggle the value of 'clock' at every half-cycle (1 clock period = 20).
    // 'always' statement is continuously repeated.
    always begin
        #10 clock = ~clock;
        $display("current time: %d, value of the clock: %b", $time, clock)
    end

    // 'initial' statement is executed at the beginning of the simulation (time 0).
    // However, '$finish' is executed at time 1000.
    // '$finish' stops simulation.
    initial begin
        #1000 $finish;
    end

endmodule
```

Behavioral modeling

- Timescale (`timescale)

```
`timescale 1ns (time measurement) / 10ps (precision)
```

```
#2: 2 ns (o)
```

```
#2.2: 2.2 ns (o)
```

```
#2.22: 2.22 ns (o)
```

```
#2.222: 2.222 ns (x): because precision can be rounded off up to 10 ps
```

- Delay (#time)

- Intra delay assignment
- Regular delay assignment
- Block assignment (=): executed in the ordered of program code
- Non-blocking assignment (<=): executed concurrently

Behavioral modeling

- Delay (#time)
 - Intra delay assignment
 - Inter delay assignment
 - Block assignment (=): executed in the ordered of program code
 - Non-blocking assignment (<=): executed concurrently

```
initial begin
    x = 0; y = 1; z = 1; // time 0
    count = 0; // time 0
    reg_a = 16'b0; reg_b = reg_a; // time 0

    #15 reg_a[2] = 1'b1; // time 15
    #10 reg_b[15:13] = {x, y, z} // time 25

    count = count + 1;
end
```

```
always begin
    x = 0; y = 1; z = 1; // time 0
    count = 0; // time 0
    reg_a = 16'b0; reg_b = reg_a; // time 0

    reg_a[2] <= #15 1'b1; // time 15
    reg_b[15:13] <= #10 {x, y, z} // time 10

    count = count + 1; // time 0
end
```

Behavioral modeling

- Procedural assignment (updating values) with **always**

- Always statement:

```
always @(sensitivity list) begin
    ...
end
```

- Sensitivity list: The list of events or signals expressed as an OR

- Combinational logic (asynchronous)

```
module comb_logic(input x, input y, output z);
```

```
reg reg_z;
```

```
assign z = reg_z;
```

```
always @(x or y) begin
    reg_z = x & y;
end
```

} Always statement is triggered
whenever one of x and y is changed.

```
endmodule
```

```
module comb_logic(input x, input y, output z);
```

```
reg reg_z;
```

```
assign z = reg_z;
```

```
always @(*) begin
    reg_z = x & y;
end
```

} '*' implies x and y

```
endmodule
```

'reg_z' must be declared by 'reg'

* lvalue inside always statement must be one of reg, integer, real, and time register

Behavioral modeling

- Procedural assignment with **always**
 - Always statement:

```
always @(sensitivity list) begin  
    ...  
end
```

- Sensitivity list: The list of events or signals expressed as an OR

- Combinational logic (asynchronous)

```
module comb_logic(input sel, input a, input b,  
                  output z);
```

```
    reg reg_z;
```

```
    assign z = reg_z;
```

```
    always @(*) begin  
        if (sel)  
            reg_z = a;  
        else  
            reg_z = b;  
    end
```

```
endmodule
```

```
module comb_logic(input sel, input a, input b,  
                  output z);
```

```
    reg reg_z;
```

```
    assign z = reg_z;
```

```
    always @(*) begin  
        case (sel)  
            0 : reg_z = b;  
            1 : reg_z = a;  
            default: reg_z = 1'b1  
        end
```

```
endmodule
```

Be careful! Default condition must exist (e.g., else in if-else, default in case)

Behavioral modeling

- Procedural assignment with **always**

- Always statement:

```
always @(sensitivity list) begin  
    ...  
end
```

- Sensitivity list: The list of events or signals expressed as an OR

- Synchronous logic

```
module counter(input clk);  
  
    reg [31 : 0] counter;  
  
    always @(posedge clk) begin  
        counter <= counter + 1;  
    end  
  
endmodule
```

```
module swap_non_blocking(input clk, ...);
```

```
    always @(posedge clk) begin  
        a <= b;  
    end
```

```
    always @(posedge clk) begin  
        b <= a;  
    end
```

```
endmodule
```

1. What will be the type (wire or reg) of a and b?
2. Are always statements executed in the order?
3. What happen to a and b?

Behavioral modeling

- Procedural assignment with **always**

- Always statement:

```
always @(sensitivity list) begin  
    ...  
end
```

- Sensitivity list: The list of events or signals expressed as an OR

- Non-blocking vs blocking

```
module swap_non_blocking(input clk, ...);
```

```
    always @(posedge clk) begin  
        a <= b;  
    end
```

```
    always @(posedge clk) begin  
        b <= a;  
    end
```

```
endmodule
```

Non-blocking

```
module swap_blocking(input clk, ...);
```

```
    always @(posedge clk) begin  
        a = b;  
    end
```

```
    always @(posedge clk) begin  
        b = a;  
    end
```

```
endmodule
```

Blocking

1. What happen to a and b?

Behavioral modeling

- Procedural assignment with **always**

- Always statement:

```
always @(sensitivity list) begin  
    ...  
end
```

- Sensitivity list: The list of events or signals expressed as an OR

- Synchronous write, asynchronous read memory

```
module mem(clk, wr_en, wr_addr, rd_addr, in_data, ret_data);  
    localparam data_width = 512;  
    localparam size = 1024;  
  
    input clk, wr_en;  
    input [size - 1] wr_addr;  
    input [size - 1] rd_addr;  
    input [data_width - 1] in_data;  
    output [data_width - 1] ret_data;  
  
    reg [data_width - 1 : 0] mem[size - 1 : 0];  
  
    assign ret_data = mem[rd_addr]; // asynchronously read data  
    always @(posedge clk) begin  
        if (wr_en)  
            mem[wr_addr] <= in_data; // synchronously write data  
        end  
    endmodule
```

wire vs reg

- Rules for picking a wire or reg net type:
 - If a signal needs to be assigned inside an always block, it must be declared as a reg
 - If a signal is assigned using a continuous assignment statement, it must be declared as a wire
 - If any output ports in the port declaration are assigned in an always block, they must be declared as output reg
 - module a (input a, input b, output reg c); ... endmodule
- How to know if a type of variable represents a register or a wire ?
 - A wire always represents a combinational link
 - A reg represents a wire if it is assigned in an always @(*) block
 - A reg represents a register if it is assigned in an always @(posedge / negedge sth) block

References

- https://inst.eecs.berkeley.edu/~eecs151/fa19/files/verilog/Verilog_Primer_Slides.pdf
- <http://courses.csail.mit.edu/6.111/f2004/handouts/L04.pdf>
- https://d1.amobbs.com/bbs_upload782111/files_33/ourdev_585395BQ8J9A.pdf